

BASIC ELECTRONICS

(24B11EC111)

Unit-1

Lecture-7

(Superposition Theorem)

CONTENTS

- **Network Theorems**
- **Linearity Property**
- **Superposition Theorem**
- **Problem**
- **References**

Network Theorems

- To handle the complex circuits, engineers have developed some theorems like Superposition Theorem, Thevenin's Theorem, Norton's Theorem, Maximum Power Transfer Theorem, Source Transformation.
- Since these theorems are applicable to linear circuits, we first discuss the concept of circuit linearity.

Linearity Property

- Linearity is the property of an element describing a linear relationship between cause and effect.
- The property is a combination of both the **homogeneity (scaling)** property and the **additivity** property.
- The **homogeneity property** requires that if the **input is multiplied by a constant**, then the **output is multiplied by the same constant**.
- The **additivity property** requires that the **response to a sum of inputs is the sum of the responses to each input applied separately**.
- **Resistor is a linear element** because the **voltage-current relationship** satisfies both the **homogeneity** and the **additivity** properties.
- In general, a circuit is linear if it is both additive and homogeneous.
- A **linear circuit** consists of only **linear elements, linear dependent sources, and independent sources**.

Superposition Theorem


- ❖ The **superposition** principle states that **the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.**
- **To apply** the superposition principle, we must keep **two things** in mind:
 1. We consider **one independent source at a time** while all **other independent sources are turned off**. This implies that we replace **every voltage source by 0 V (or a short circuit)**, and every **current source by 0 A (or an open circuit)**. This way we obtain a simpler and more manageable circuit.
 2. **Dependent sources** are **left intact** because they are **controlled by circuit variables**.

Superposition Theorem

- **With these in mind, we apply the superposition principle in three steps:**
 1. **Turn off all independent sources except one source. Find the output (voltage or current) due to that active source.**
 2. **Repeat** step 1 for each of the other independent sources.
 3. Find the **total contribution by adding algebraically all the contributions due to the independent sources.**

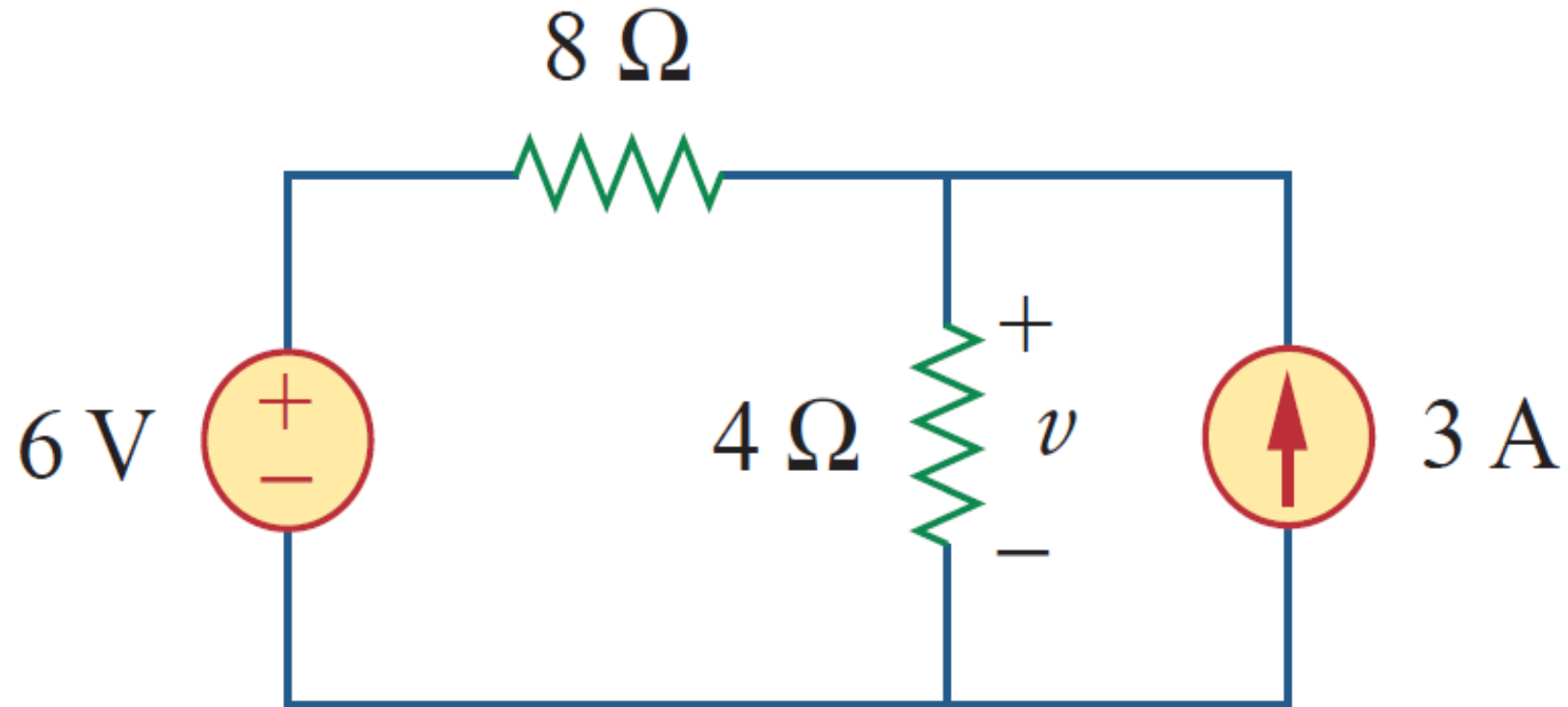Problem

Use the superposition theorem to find v in the circuit of Fig.



Problem - Solution

Since there are two sources, let

$$v = v_1 + v_2$$

where v_1 and v_2 are the contributions due to the **6-V voltage source** and the **3-A current source**, respectively.



To obtain v_1 we set the **current source to zero**, as shown in Figure.

$$12i_1 - 6 = 0 \quad \Rightarrow \quad i_1 = 0.5 \text{ A}$$

Applying KVL to the loop gives

Thus



$$v_1 = 4i_1 = 2 \text{ V}$$

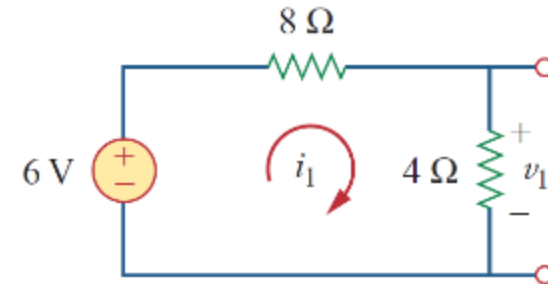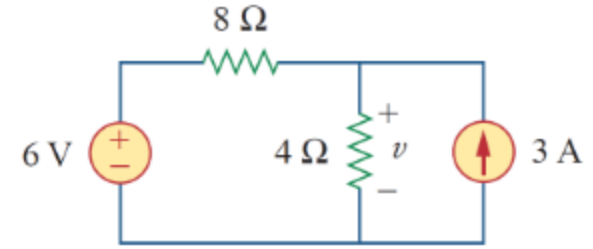

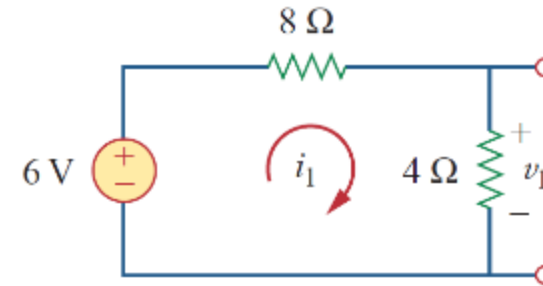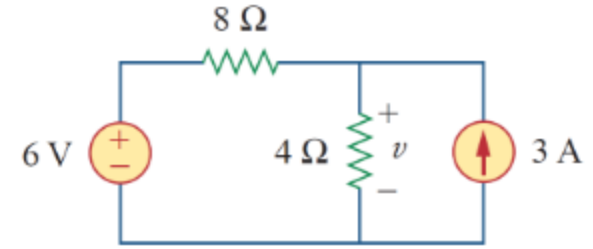Problem - Solution

We may also use voltage division to get v_1 by writing

$$v_1 = \frac{4}{4 + 8}(6) = 2 \text{ V}$$



Problem - Solution

To get v_2 we set the voltage source to zero, as in Figure.



Using current division,

$$i_3 = \frac{8}{4 + 8}(3) = 2 \text{ A}$$

Hence,


$$v_2 = 4i_3 = 8 \text{ V}$$

And we find
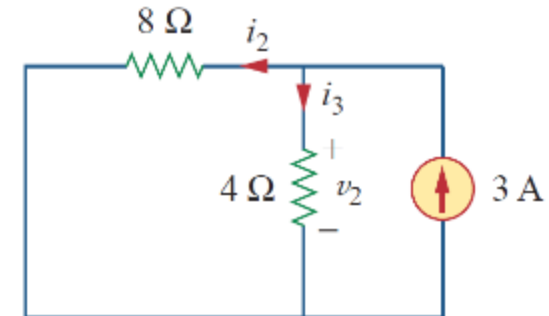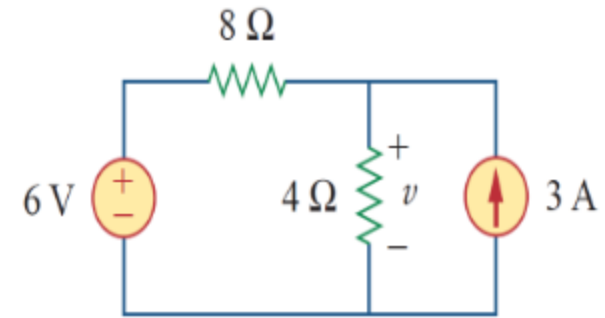
$$v = v_1 + v_2 = 2 + 8 = 10 \text{ V}$$

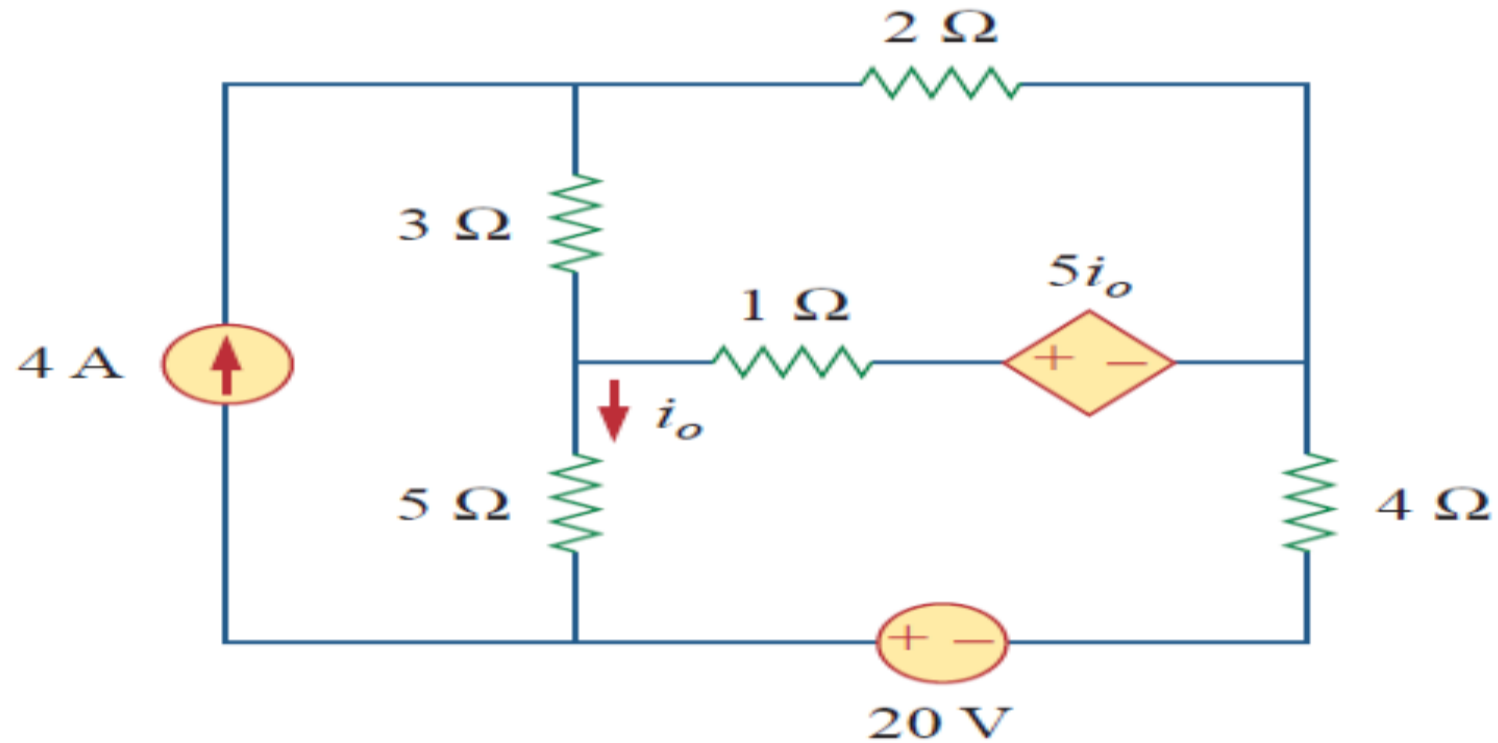
Problem

Find i_o in the circuit of Figure using superposition.



Problem - Solution

The circuit in Figure involves a **dependent source**, which must be left intact.

We let

$$i_o = i'_o + i''_o$$

where i'_o and i''_o are due to the **4-A current source** and **20-V voltage source** respectively.

To obtain i'_o we **turn off the 20-V source (short circuit)** so that we have the circuit in Figure.



We apply mesh analysis in order to obtain

For loop 1,

$$i_1 = 4 \text{ A}$$

For loop 2,

$$-3i_1 + 6i_2 - 1i_3 - 5i'_o = 0$$

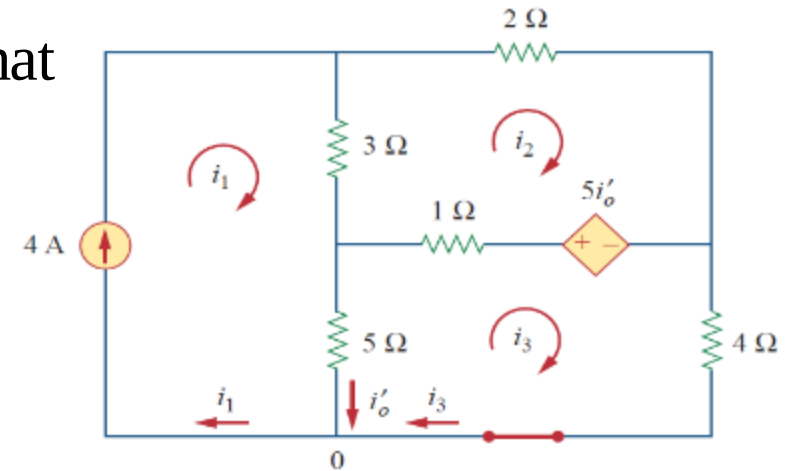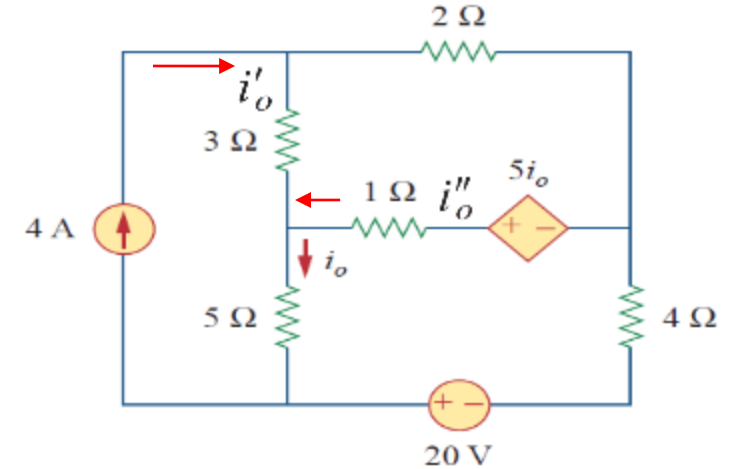

Problem - Solution

For loop 3,

$$-5i_1 - 1i_2 + 10i_3 + 5i'_o = 0$$

But at node 0,

$$i_3 = i_1 - i'_o = 4 - i'_o$$


By substituting, we get

$$3i_2 - 2i'_o = 8$$

$$i_2 + 5i'_o = 20$$

After solving, we get

$$i'_o = \frac{52}{17} \text{ A}$$

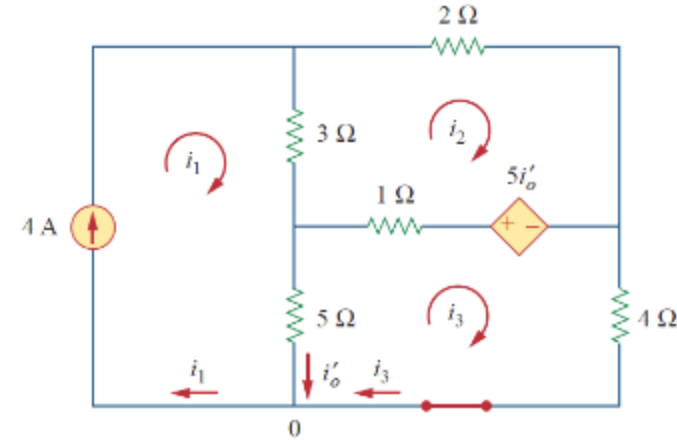

Problem - Solution

To obtain i_o'' we turn off the 4-A current source so that the circuit becomes that shown in Figure.

For loop 4, KVL gives

$$6i_4 - i_5 - 5i_o'' = 0$$

and for loop 5,

$$-i_4 + 10i_5 - 20 + 5i_o'' = 0$$

But

$$i_5 = -i_o''$$

Substituting this in Equations gives

$$6i_4 - 4i_o'' = 0$$

$$i_4 + 5i_o'' = -20$$


which we solve to get

$$i_o'' = -\frac{60}{17} \text{ A}$$

Finally, we get


$$i_o = i_o' + i_o''$$
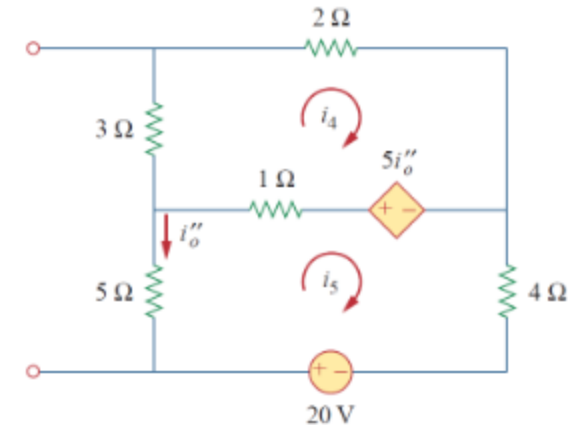
$$i_o = -\frac{8}{17} = -0.4706 \text{ A}$$



Practice Problem

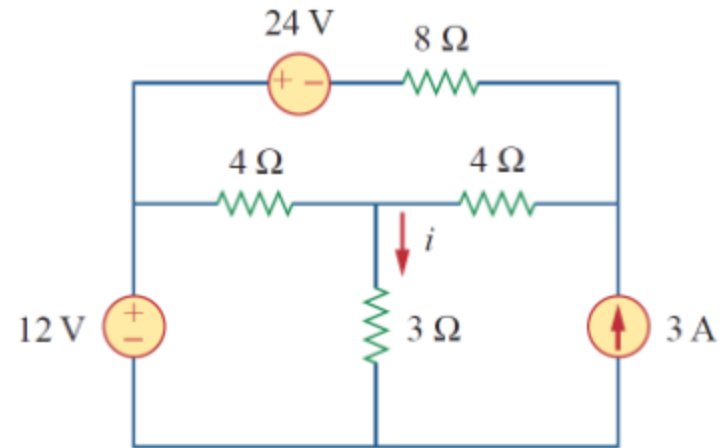For the circuit in Figure, use the superposition theorem to find i .



Ans: 2 A

References

1. R.C. Dorf and James A. Svoboda, "Introduction to Electric Circuits", 9th ed, John Wiley & Sons, 2013.
2. D.C. Kulshreshtha, Basic Electrical Engineering, Revised 1st ed, Tata Mc Graw Hill, 2017.
3. V. K.Mehta, Rohit Mehta, Basic Electrical Engineering, 6th ed, S. Chand Publishing, 2012.